

## Norton's Thm:

- Norton's theorem is used for simplifying a network in terms of currents instead of voltages. According to this theorem, any complicated network can be replaced by equivalent circuit consisting of
  - an ideal current source ( $I_N$ ) of infinite internal resistance and
  - a resistance ( $R_N$ ) in parallel with it as shown in Fig. 1.24.

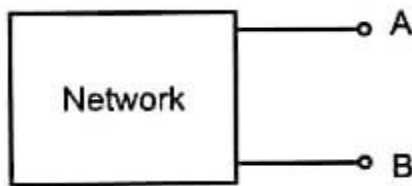


Fig. 1.23


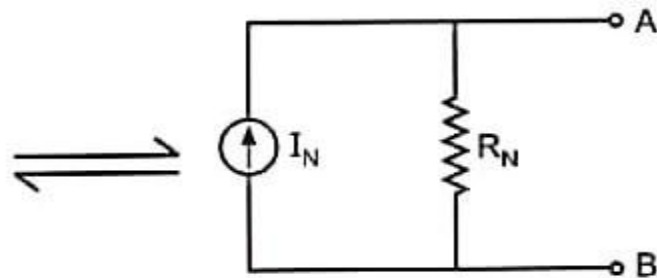



Fig. 1.24 : Norton's equivalent circuit

**Statement :** Any two-terminal linear network, containing sources of e.m.f. and resistances, can be replaced by an equivalent circuit consisting of constant current source ( $I_N$ ) in parallel with a single resistance ( $R_N$ ). The constant current is equal to the current which would pass in a short circuit placed between the terminals and  $R_N$  is the resistance between the terminals when all the sources in the network have been replaced by their internal resistances.

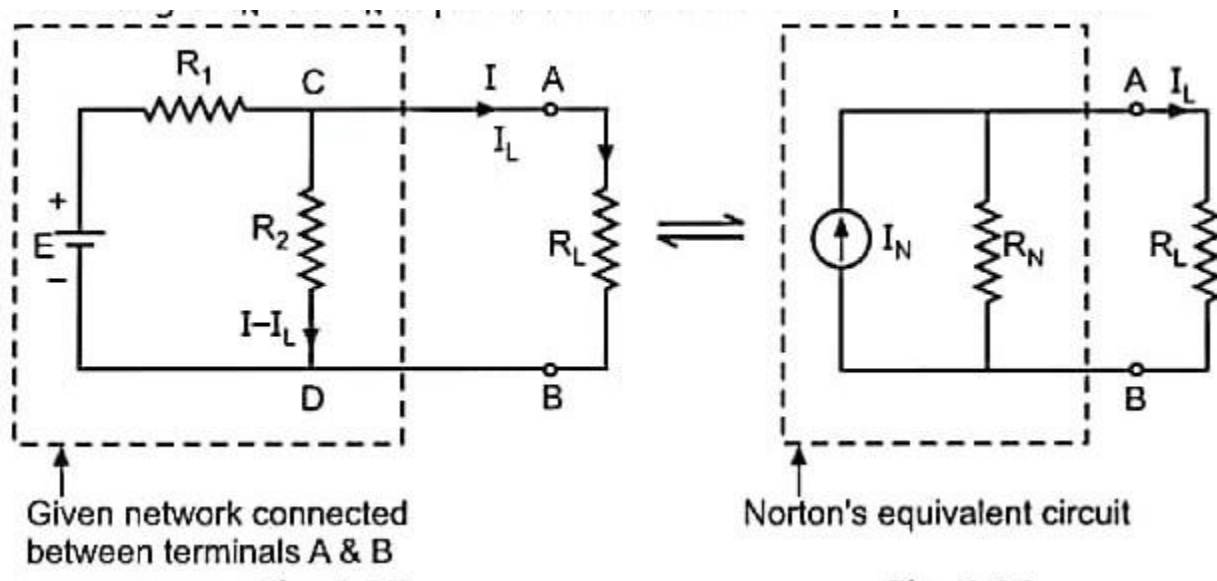

## How to Nortonize a given circuit ?

To understand how to Nortonize a given circuit, consider the following circuit shown in Fig. 1.29.

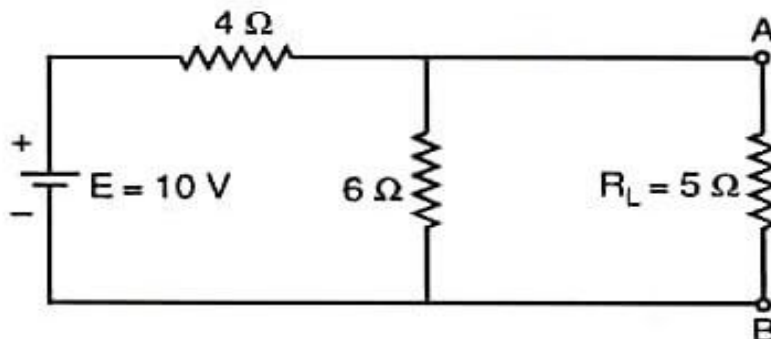


**Fig. 1.29**

The procedural steps for finding Norton's equivalent circuit are as under.

**Step I :** Disconnect the load resistor  $R_L = 5 \Omega$  from the terminals A and B.

**Step II :** To find Norton's current, put a short across the terminals A and B. It results in shorting out  $6 \Omega$  resistor as shown in Fig. 1.30. Now the entire battery current flows through the short circuit.

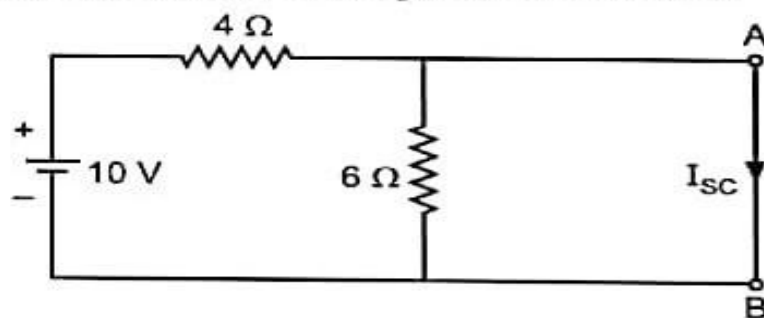


**Fig. 1.30**

$$I_{sc} = \frac{10 \text{ volts}}{4 \Omega} = 2.5 \text{ A}$$

This current is also called Norton's current ( $I_N$ ).

$$\therefore I_N = 2.5 \text{ A}$$

**Step III :** Remove the short from terminals A and B, so that they are again open. To find  $R_{eq}$ , remove the battery and replace it by its internal resistance (in this case it is zero). The equivalent resistance ( $R_{eq}$ ) is also known as Norton's resistance  $R_N$  of the circuit viewed back from open terminals A and B as shown in Fig. 1.31.

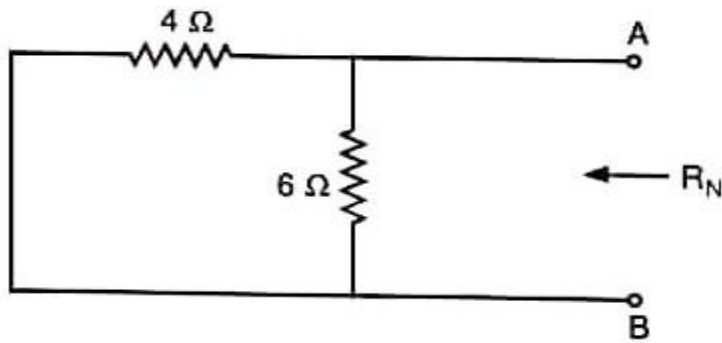


**Fig. 1.31**

$$R_N \text{ or } R_{eq} = \frac{4 \times 6}{4 + 6} \quad (\because 4 \Omega \parallel 6 \Omega)$$

$$\therefore R_{eq} = 2.4 \Omega$$


$$\text{Or } R_N = 2.4 \Omega$$

The Norton's equivalent of the given circuit consists of a 2.5 A constant current source in parallel with a 2.4  $\Omega$  resistance. (Refer Fig. 1.32)

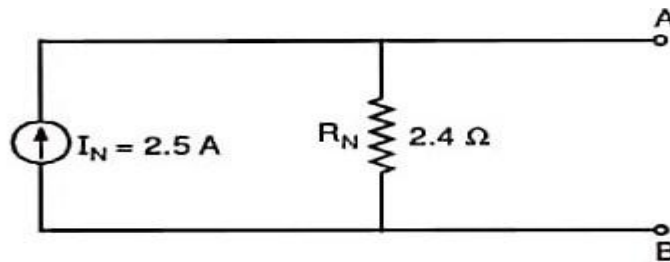

**Fig. 1.32 : Norton's equivalent circuit**

**Step IV :** Load current  $I_L$  passing through  $R_L = 5 \Omega$  can be obtained by using the proportional current formula.

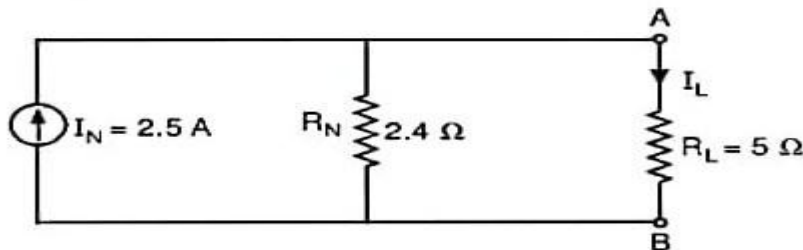

**Fig. 1.33**

From Fig. 1.33, the current passing through  $R_L$  is

$$I_L = I_N \times \frac{R_N}{(R_N + R_L)}$$


$$I_L = 2.5 \times \frac{2.4}{2.4 + 5}$$

$$I_L = 0.81 \text{ A}$$

**Problems:1**

**(Ans.  $V_{Th} = 18\text{ V}$ ,  $R_{Th} = 3\ \Omega$ )**

Using Norton's theorem, calculate the current flowing through  $12\ \Omega$  resistor as shown in Fig. 1.75.

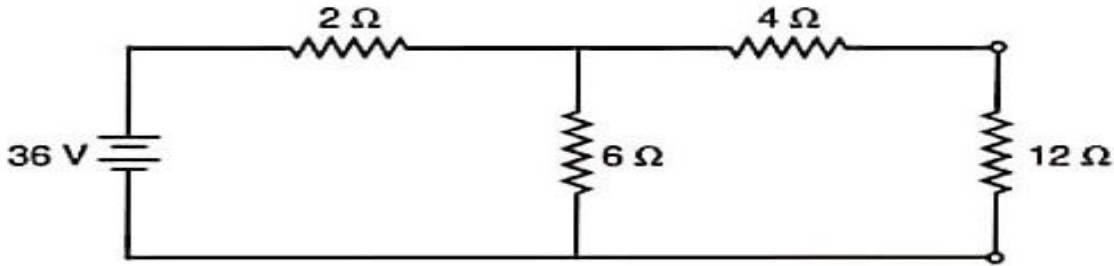


**Fig. 1.75**

**(Ans.  $I_L = 1.54\text{ A}$ )**

**Problems:2**

Nortonize the following circuit and calculate current across  $8\ \Omega$  resistor.

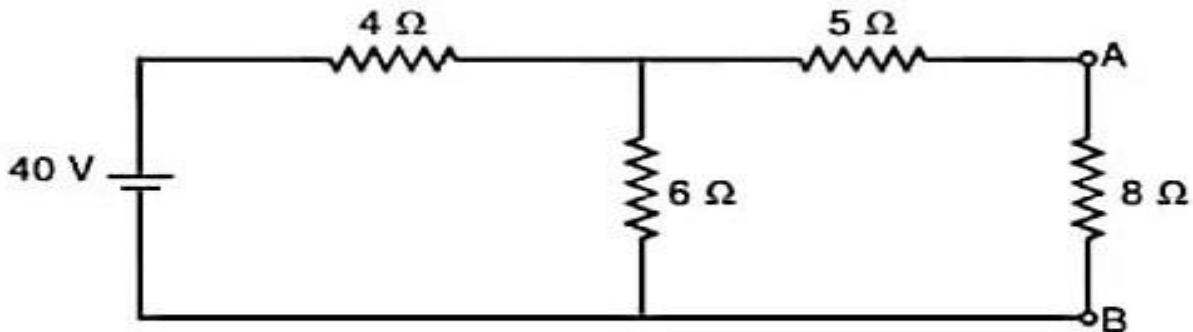

**Fig. 1.76**

**(Ans.  $I_N = 3.24\text{ A}$ ,  $R_N = 7.4\ \Omega$ ,  $I_L = 1.55\text{ A}$ )**